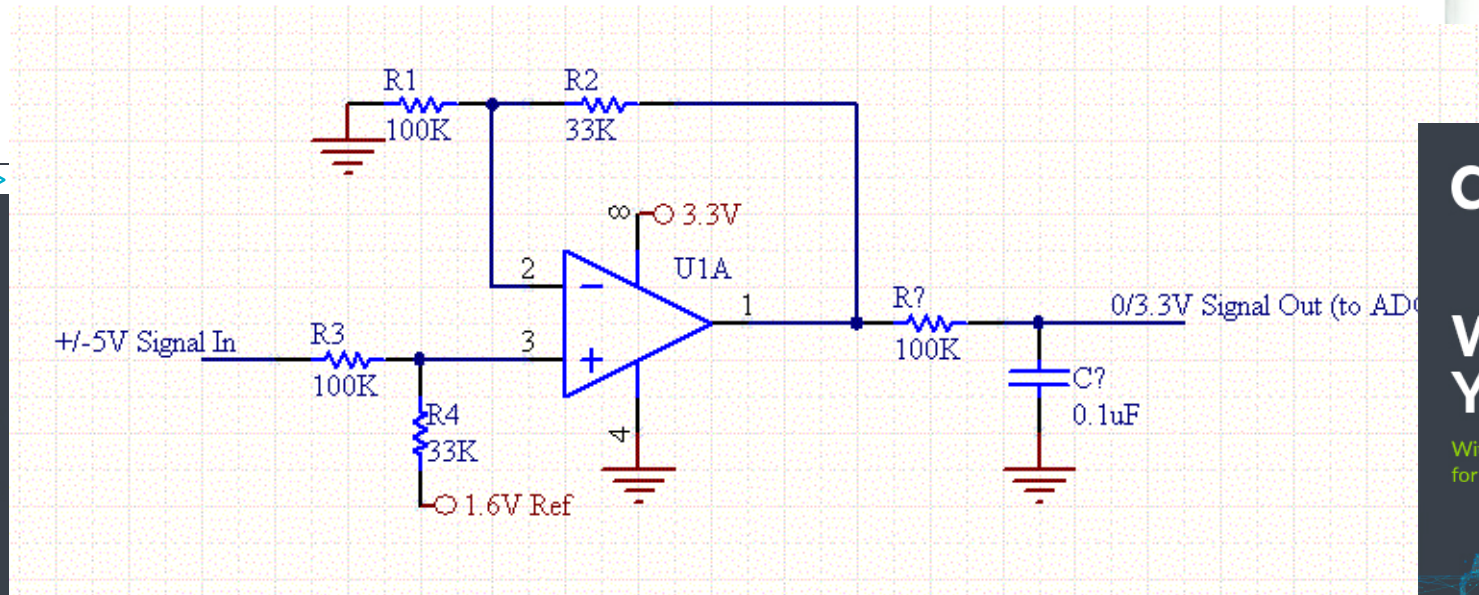
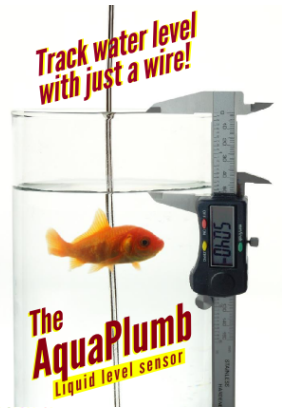




# Non-Inverting Op-Amp Level Shifter

A common engineering task is to convert a positive to negative signal into a range suitable for a single supply ADC. This circuit will convert a +/-5V signal into a 0 to 3.3V signal so that it can be sampled by an ADC on a 3.3V microprocessor.



Check out our [Op-Amp Resistor-Calculator](#).

## Equations:

$$A = (R4/R1) \times (R1+R2)/(R3+R4)$$

If  $R1 = R3$ , and  $R2 = R4$ , then

$$A = (R4/R1)$$

We want to convert a 10Vpp signal to a 3.3V signal so the gain should be 1/3. We can choose  $R4$  to be 33K and  $R1$  to be 100K.

Now we need to choose the positive offset such that the signal is centered at 1.6V.

The gain off the offset voltage is:

$$A_{\text{offset}} = (R2+R1)/R1 \times R3/(R3+R4) = R3/R1.$$

For the previous resistor values, the gain is 1 since  $R3 = R1$ , and so we use an offset voltage of 1.6V.

